
Signal Conditioning and Data Processing

To complete the whole system design, integration of individual parts was the first on the list of things to be done. There are following individual modules have been developed:

 - 1. Signal conditioning circuit using two instrumentation amplifiers (INA129)
- 2. Power supply circuit to get dual power supply (+15 V and -15 V) from 220 V AC supply
- 3. Power supply circuit to get +7V for load cell
- 4. Microcontroller ATmega for analog to digital conversion of output obtained after signal conditioning
- 5. LCD to display any alphanumeric characters (interfaced using the microcontroller)

The initial task was to combine the individual modules number 4 and 5 mentioned above (i.e. to display the digital converted value on LCD)

The following diagram shows LCD connections to the microcontroller (We are using a 16 x 2 LCD for our purpose):



To simply run the LCD using the ATmega 2560 microcontroller, the following code was used:

#include <LiquidCrystal.h>

```
// initialize the library with the numbers of the interface pins LiquidCrystal Icd(48,46,44,42,40,38,36,34,32,30,28); void setup() {
    // set up the LCD's number of columns and rows: pinMode(52, OUTPUT); // set pin to OUTPUT digitalWrite(52, HIGH); pinMode(50, OUTPUT); // set pin to OUTPUT digitalWrite(50, LOW);// turn on pullup resistors Icd.begin(16, 2);
```

```
// Print a message to the LCD.
 lcd.print("a"); //display any value
 lcd.setCursor(0, 1);
 Icd.print("bb"); //display any value in the next line
void loop() {
}
Now, to decrease the number of pins used and also switch on the backlight of the LCD the
following code was used:
#include <LiquidCrystal.h>
// initialize the library with the numbers of the interface pins
LiquidCrystal lcd(48,44,34,32,30,28); //Only 4 data pins used now
void setup() {
 // set up the LCD's number of columns and rows:
 pinMode(52, OUTPUT);
                           // set pin to OUTPUT
 digitalWrite(52, HIGH);
 pinMode(46, OUTPUT); // set pin to OUTPUT
 digitalWrite(46, LOW);
                           //RS pin is also grounded in this case of 4 data pins
 pinMode(50, OUTPUT);
                            // set pin to OUTPUT
 digitalWrite(50, LOW);// turn on pullup resistors
 Icd.begin(16, 2);
 // Print a message to the LCD.
 lcd.print("a"); //display anything
 lcd.setCursor(0, 1);
 lcd.print("bb"); //display anything
 //setting backlight
 pinMode(24, OUTPUT);
                             // set pin to OUTPUT
 digitalWrite(24, LOW);
 pinMode(26, OUTPUT);
                           // set pin to OUTPUT
 digitalWrite(26, HIGH);
void loop() {
}
```

Using the above code, the LCD was now glowing it's backlight and also only 4 data pins were being utilised to display anything to the LCD. Now, to combine this code with the ADC

code previously developed, some modifications were made. Now, number 4 and number 5 modules mentioned above have been combined.

```
#include <LiquidCrystal.h>
LiquidCrystal Icd(48,44,34,32,30,28); //using 4 data pins d4-d7.
//RW is gnd, RS and EN are in the func.
void setup() {
 // initialize serial communication at 9600 bits per second:
 Serial.begin(9600);
       // set up the LCD's number of columns and rows:
 pinMode(52, OUTPUT);
                            // set pin to OUTPUT
 digitalWrite(52, HIGH);
 pinMode(46, OUTPUT):
                            // set pin RS to OUTPUT and GND
 digitalWrite(46, LOW);
 pinMode(50, OUTPUT);
                            // set pin to OUTPUT
 digitalWrite(50, LOW);
 //setting backlight
 pinMode(24, OUTPUT);
                            // set pin to OUTPUT
 digitalWrite(24, LOW);
 pinMode(26, OUTPUT);
                            // set pin to OUTPUT
 digitalWrite(26, HIGH);
}
// the loop routine runs over and over again forever:
void loop() {
 weight= 1.027*analogRead(inputPin); 1.027 is the slope obtained from readings
(Calibration //factor)
 // add the reading to the total:
 Serial.println(weight);
 Icd.begin(16, 2);
 // Print a message to the LCD.
 lcd.print(weight);
 lcd.setCursor(5, 0);
 lcd.print(grams);
 delay(2); // delay in between reads for stability
}
```

The sampling rate of the ADC is very fast and hence the values being displayed change continuously and are not visible statically for better aesthetic display to the user. Also, the readings are not very accurate and change continuously. Hence, we proposed the solution to this problem in terms of a moving average filter.

This moving average filter would make the values more stable on the display and also this would provide for post-processing of the data that we are obtaining through the signal conditioning and digital conversion. This post processing is done by taking a moving average of a fixed number of samples. This improved the final result and the output value of the weight as well. The following code implements the moving average filter and can be considered as the final code that can be used for weight measurement and display system.

```
#include <LiquidCrystal.h>
const int numReadings = 10;
int readings[numReadings]; // the readings from the analog input
int readIndex = 0:
                            // the index of the current reading
int total = 0:
                    // the running total
int average = 0;
                            // the average
int inputPin = A0;
// initialize the library with the numbers of the interface pins
LiquidCrystal Icd(48,44,34,32,30,28); //using 4 data pins d4-d7.
//RW is gnd, RS and EN are in the func.
void setup() {
 // initialize serial communication at 9600 bits per second:
 Serial.begin(9600);
       // set up the LCD's number of columns and rows:
 pinMode(52, OUTPUT);
                           // set pin to OUTPUT
 digitalWrite(52, HIGH);
 pinMode(46, OUTPUT); // set pin RS to OUTPUT and GND
 digitalWrite(46, LOW);
 pinMode(50, OUTPUT):
                            // set pin to OUTPUT
 digitalWrite(50, LOW);// turn on pullup resistors
 for (int thisReading = 0; thisReading < numReadings; thisReading++) {
       readings[thisReading] = 0;
 }
 //setting backlight
 pinMode(24, OUTPUT);
                            // set pin to OUTPUT
 digitalWrite(24, LOW);
 pinMode(26, OUTPUT);
                           // set pin to OUTPUT
```

```
digitalWrite(26, HIGH);
}
// the loop routine runs over and over again forever:
void loop() {
 // subtract the last reading:
 total = total - readings[readIndex];
 // read from the sensor:
 readings[readIndex] = 1.027*analogRead(inputPin); //1.027 is the slope obtained from
readings // (Calibration factor)
 // add the reading to the total:
 total = total + readings[readIndex];
 // advance to the next position in the array:
 readIndex = readIndex + 1:
 // if we're at the end of the array...
 if (readIndex >= numReadings) {
       // ...wrap around to the beginning:
       readIndex = 0;
 }
 // calculate the average:
 average = total / numReadings;
 // send it to the computer as ASCII digits
 Serial.println(average);
 Icd.begin(16, 2);
 // Print a message to the LCD.
 lcd.print(average);
 lcd.setCursor(5, 0);
 lcd.print(grams);
 delay(2); // delay in between reads for stability
}
```

On testing the whole setup we could obtain the weight values on the LCD successfully.


Next.

Soldering the power supply circuit to supply the following voltages:

 - a. +15V for INA129 positive supply
- b. -15V for INA129 negative supply
- c. +7V for load cell and micrcontroller supply


IC7812 and IC7912 were used respectively for the two voltages. These voltage regulator ICs provide constant voltage and can supply a maximum current of 1.2A. These specifications

are suitable for our instrumentation application of weight measurement using load cell.




In the above diagram, C1 and C2 are polar capacitances of value 1000uF and C3 and C4 are nonpolar of value 0.1uF. When xx=15, V+=15V and V-=-15V.

 Similar circuit using LM317 can be used to obtain any voltage between the range of 1V - 30V by adjusting the resistance. We used this to get +7V for load cell and microcontroller supply. The following circuit can be used:



 But. since we have already rectified the AC signal to get +15 DC voltage output from the first circuit, we need not rectify the signals again for +7V. So, the 15V DC output obtained in the first part can be used to supply +7V DC output using LM317. The above circuit in this case can be replaced by:



The breadboard simulation of the above circuit was done and was taken for soldering on a PCB. The following images show the soldered circuit which is yet to be tested rigorously for problems.



Possible Modifications:

- 1. Low pass filtering using RC on the output of the sensor
- 2. Decoupling the sensor by using a capacitor across its power supply
- 3. In the microcontroller code, implementing a mode filtering function to improve the stability of the readings and accuracy
- 4. Using 1.1V reference voltage so as to measure weights of lesser resolutions as well.
- 5. Implementing higher order butterworth (or other) filters to improve the stability of the data.

Conclusion:

The aim of the project was satisfied and the weights are being displayed as required. Though, accuracy and resolution improvements are to be done to make the whole system design perfectly working.